
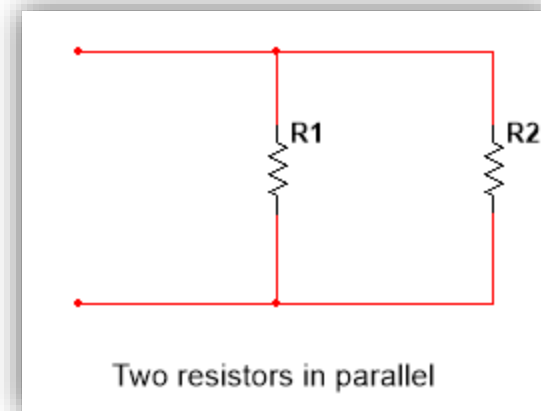


# Paramount Electronics Services

## Parallel Resistive Circuits

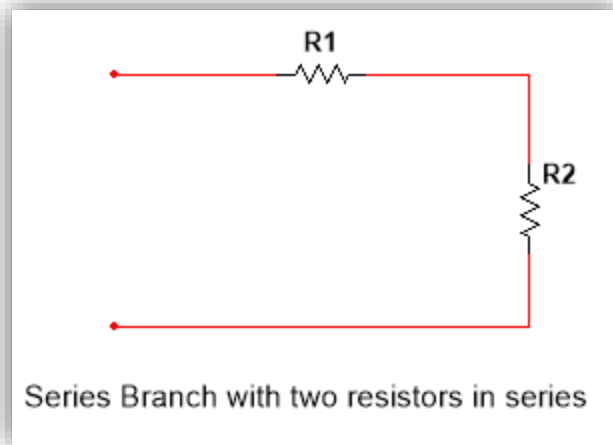
# Parallel Circuit Characteristics

- Most circuits, no matter how complex, contain components in series and/or in parallel or a combination of both.
- Sometimes however, the circuit can neither be classified as series nor parallel. This is when special circuit analysis techniques are employed.



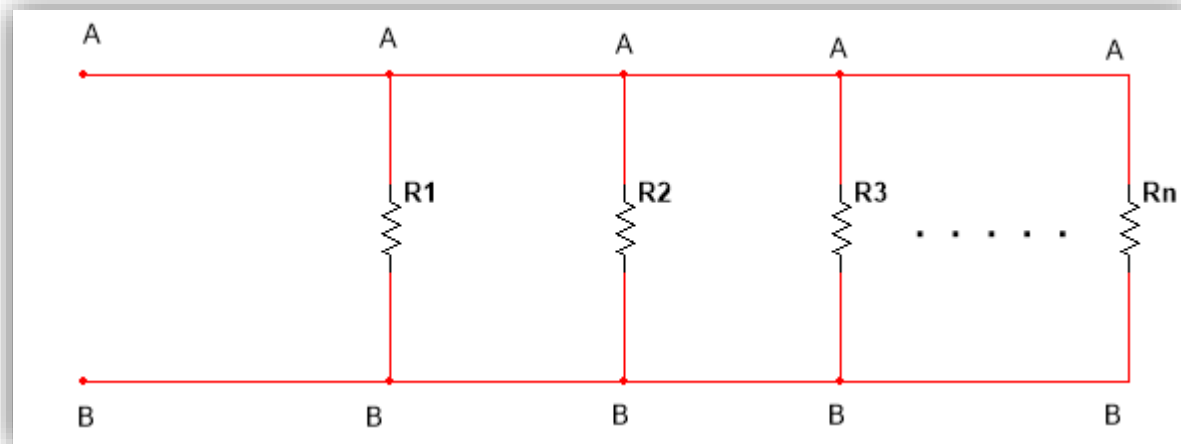
# Parallel Circuit Characteristics

- Two or more resistors are in parallel if they share two common electrical points across their terminals.
- Two nodes are the same electrical point if there are no elements between them.
- Notice in the circuit below that the two common electrical points are A & B


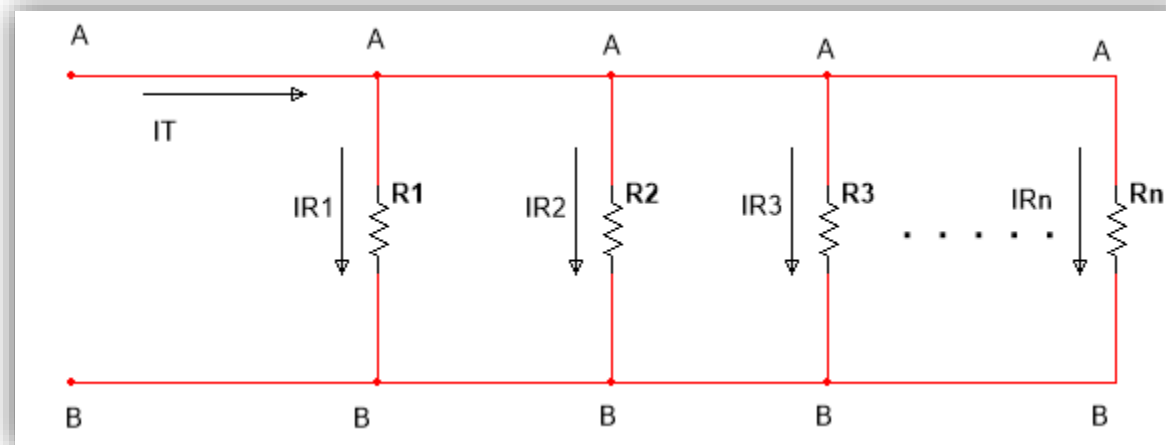
# Parallel Circuit Characteristics


- Parallel Circuit also provides more than one current path between two common points.
- Notice in the circuit below that between the two common electrical point A & B, there is  $I_{R1}$ ,  $I_{R2}$ ,  $I_{R3}$ , ....  $I_{Rn}$ .


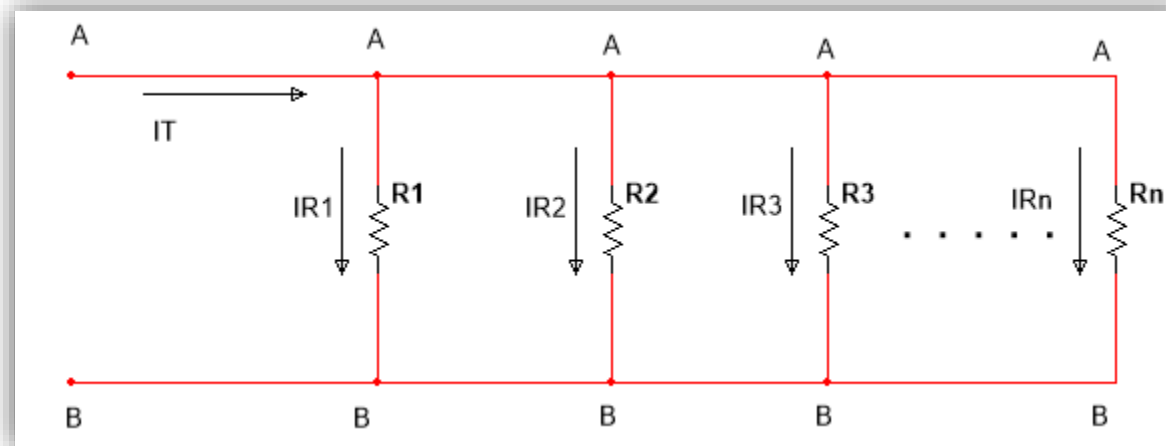
# Parallel Circuit Characteristics


- Notice in the circuit below that between the two common electrical points A & B, there is  $I_{R1}$  ,  $I_{R2}$  ,  $I_{R3}$  , ....  $I_{Rn}$  .
- Notice that the current entering Node A which is electrical point A is called  $I_T$  and it is divided between the various parallel branches.  
Therefore:

$$I_T = I_{R1} + I_{R2} + I_{R3} + .... I_{Rn}$$


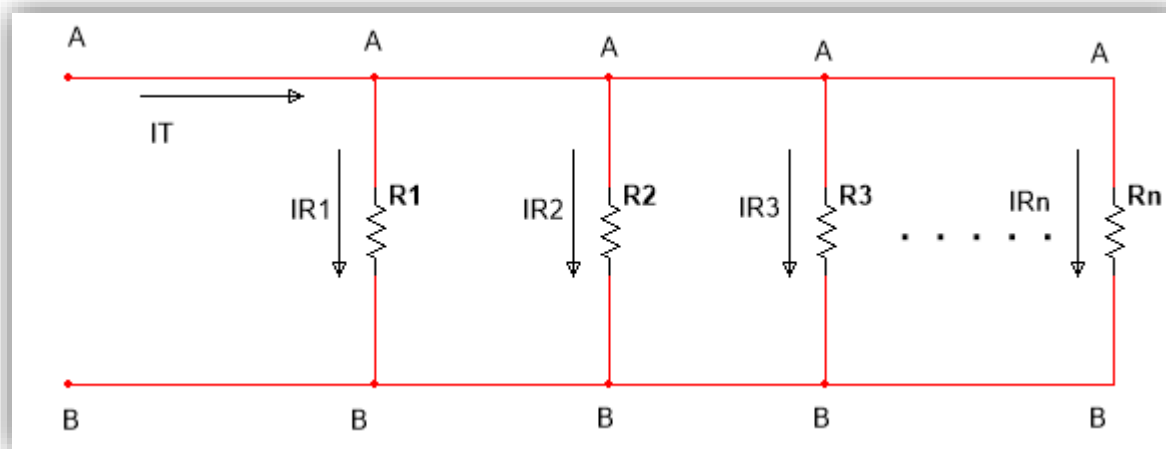
# Parallel Circuit Characteristics

- The amount of current in each branch is based on the value of the resistance of that branch.
- The higher the resistance value, the lower the current through it. The lower the resistance value the higher the current through it.
- A resistance is called as such because it resists current flow. The current flowing through a resistance and the value of that resistance are inversely proportional to each other.




## Parallel Circuit Total Resistance $R_T$

- The total resistance  $R_T$  seen between point A & B is given by the following formula:

$$R_T = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \frac{1}{R_n}\right)}$$

$$\text{If } R_1 = R_2 = R_3 = \dots R_n = R, \text{ then: } R_T = \frac{R}{n}$$

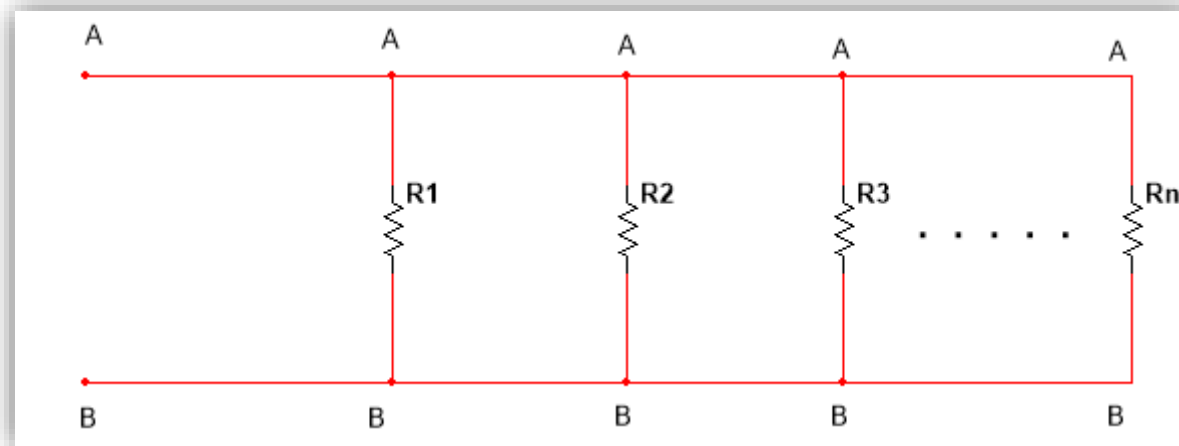- The equivalent resistance of a parallel combination will always be lower than the lowest resistance of the parallel combination.**




# Two Resistor Parallel Circuit Total Resistance $R_T$

- When only two resistors are in parallel, the reciprocal formula can still be applied, and the total resistance is given by:

$$R_T = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)}$$

- However, **only for two resistances in parallel**, the total resistance is also given by their product divided by their sum:
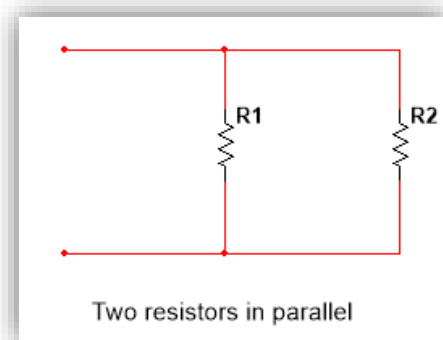
$$R_T = \frac{R_1 \times R_2}{(R_1 + R_2)}$$





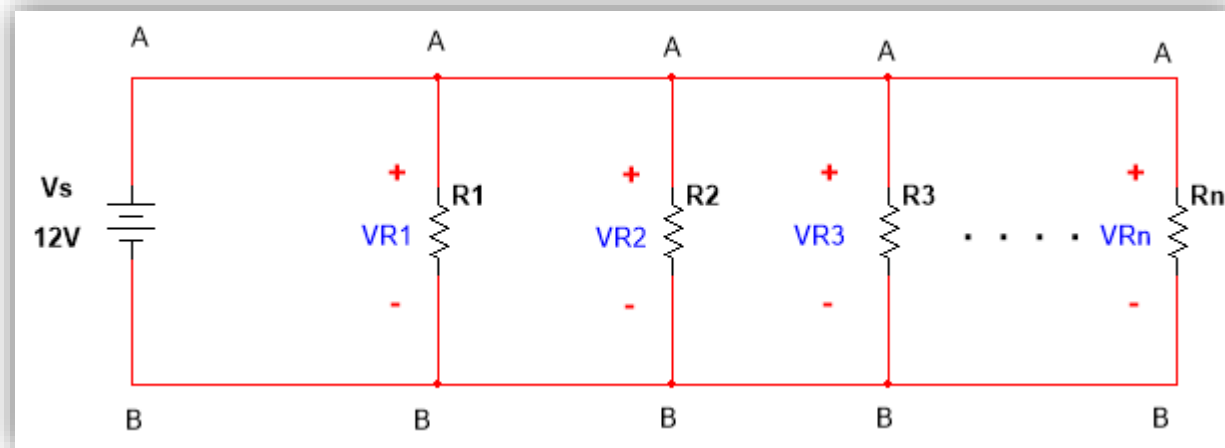
# Voltages across Elements In Parallel Circuits


- The voltage definition is the potential difference between two points.
- All elements in the parallel circuits below fall between points A and B. Therefore, the voltage across each element would be the same as the voltage between points A and B.

$$V_{AB} = V_S = V_{R1} = V_{R2} = V_{R3} = \dots V_{Rn}$$


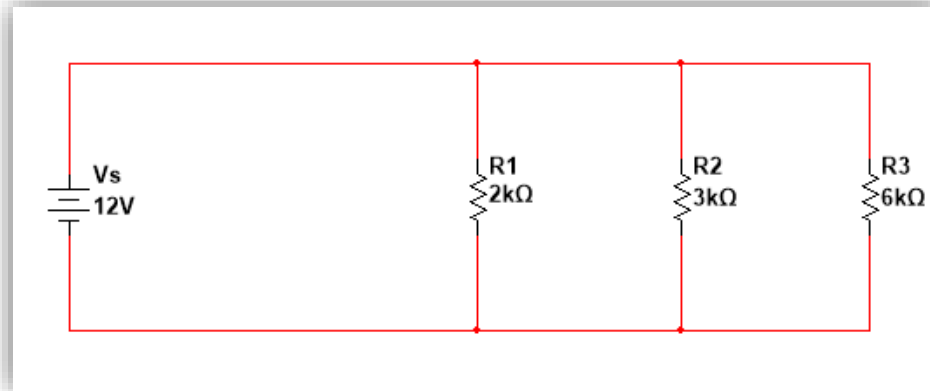
# Parallel Circuit Example

- For the following Circuit find:
  - a- Find the total resistance seen by the source
  - b- the voltages across R1, R2 & R3.
  - c- Find the currents through R1, R2 & R3
  - d- What is the total current supplied by the voltage source.
  - e - Find the power consumed by R1, R2 & R3.
  - f- Find the power delivered by the voltage source.




# Parallel Circuit Example

- For the following Circuit find:

a- Find the total resistance seen by the source

- The total resistance is given by: 
$$R_T = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)} = \frac{1}{\left(\frac{1}{2K} + \frac{1}{3K} + \frac{1}{6K}\right)} = 1K\Omega$$

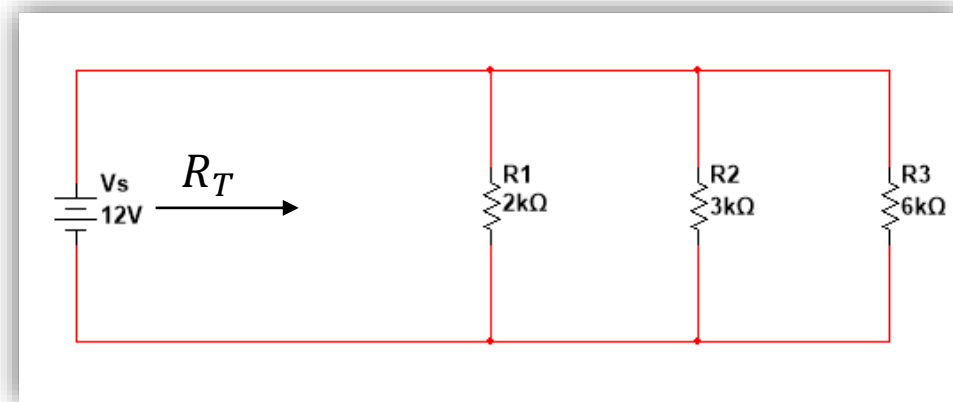
- This proves that the total resistance of 1 K is lower than the lowest resistance in the parallel branches (which is 2K).



# Parallel Circuit Example

- For the following Circuit find:
  - b- The voltages across R1, R2 & R3.
- Since all parallel branches have the same voltage across them, therefore:

$$V_S = V_{R1} = V_{R2} = V_{R3} = 12V$$

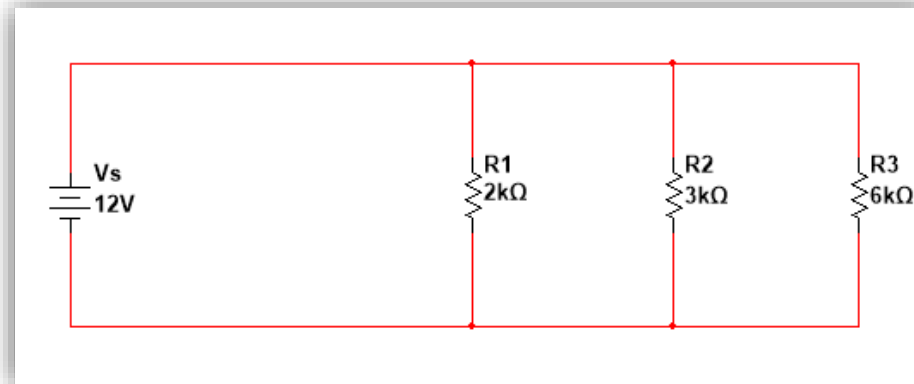

# Parallel Circuit Example

- For the following Circuit find:

c- Find the currents through R1, R2 & R3

- Using Ohm's Law, The formula used to calculate the current through a resistance is equal to the voltage across the resistance divided by the resistance. It is given by the general equation:

$$I_{Rx} = \frac{V_{Rx}}{Rx}$$

- Where:
  - $I_{Rx}$  is the current through  $Rx$ .
  - $V_{Rx}$  is the voltage across resistance  $Rx$ .
  - $Rx$  is the resistance.

# Parallel Circuit Example


- For the following Circuit find:
  - c- Find the currents through R1, R2 & R3

- Therefore:

$$I_{R1} = \frac{V_{R1}}{R1} = \frac{12\text{ V}}{2K} = 6\text{ mA}$$


$$I_{R2} = \frac{V_{R2}}{R2} = \frac{12\text{ V}}{3K} = 4\text{ mA}$$
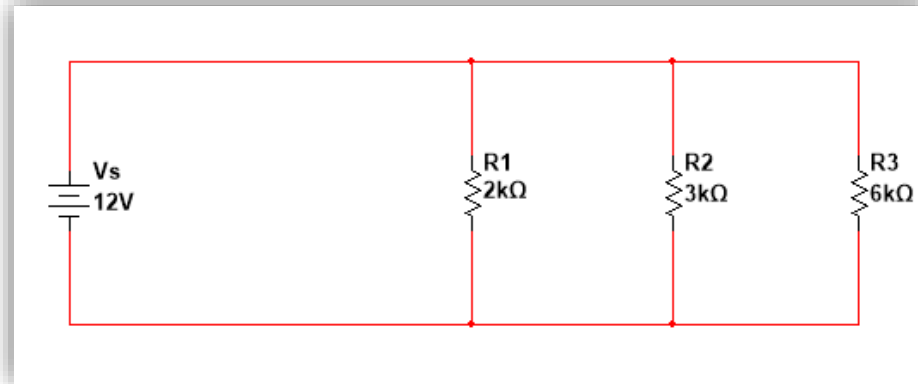
$$I_{R3} = \frac{V_{R3}}{R3} = \frac{12\text{ V}}{6K} = 2\text{ mA}$$


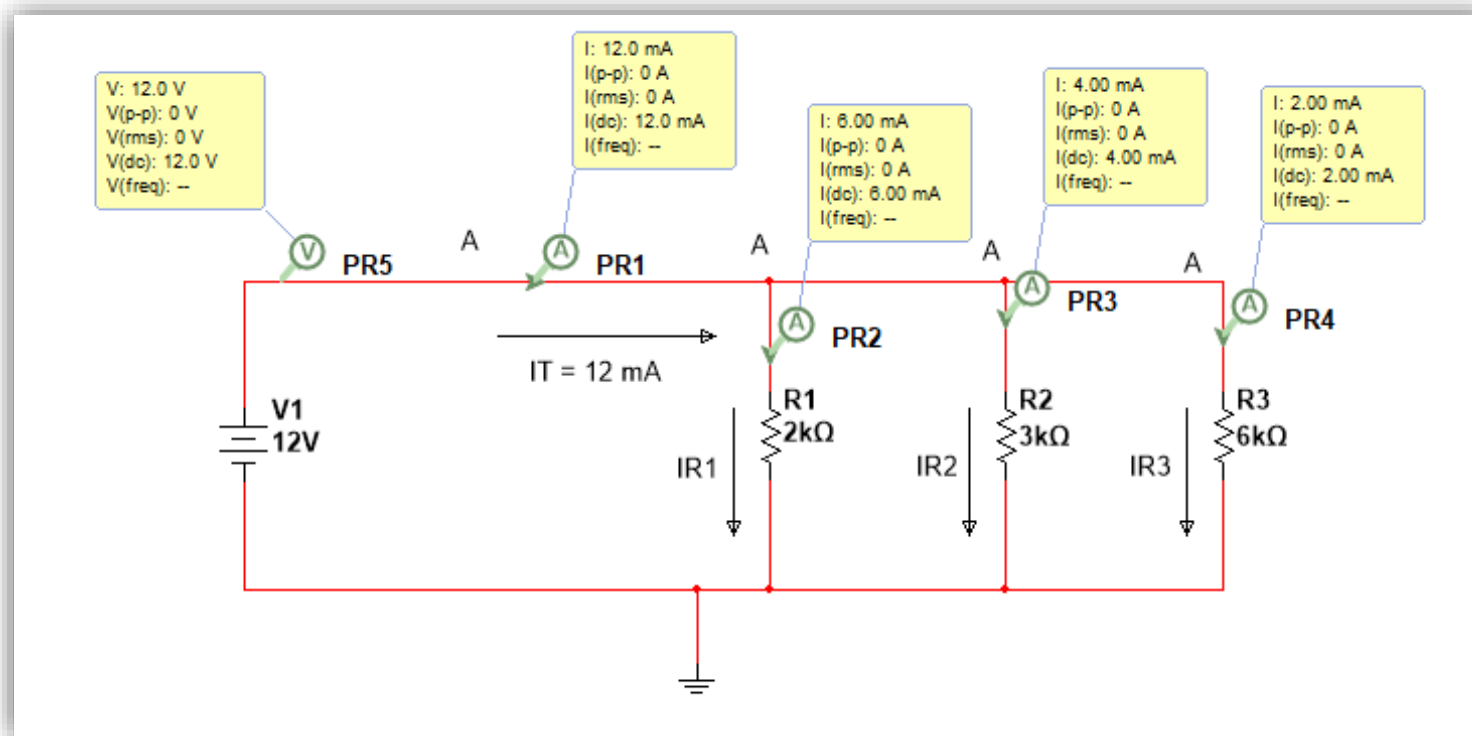
# Parallel Circuit Example

- For the following Circuit find:
  - c- Find the currents through R1, R2 & R3
- Running the simulation using MultiSim yielded the following:



# Parallel Circuit Example

- For the following Circuit find:
  - d- What is the total current supplied by the voltage source.
- The total current sourced by the voltage source is calculated either by using ohm's law:

$$I_T = \frac{V_T}{R_T} = \frac{12\text{ V}}{1\text{ K}} = 12\text{ mA}$$

- It can also be found by simply adding the individual currents flowing through the individual resistors of the parallel combination:

$$I_T = I_{R1} + I_{R2} + I_{R3} = 6\text{ mA} + 4\text{ mA} + 2\text{ mA} = 12\text{ mA}$$



# Parallel Circuit Example

- For the following Circuit find:
  - d- Find the power consumed by R1, R2 & R3.
- The Power consumed by a resistance is given by any of the following formulas:

$$P_R = V_R \times I_R$$

$$P_R = \frac{V_R^2}{R}$$

$$P_R = I_R^2 \times R$$

- Where:
  - $P_R$  is the power consumed by R.
  - $V_R$  is the voltage across R.
  - $I_R$  is the current through R.


# Parallel Circuit Example

- For the following Circuit find:
  - d- Find the power consumed by R1, R2 & R3.
- The Power consumed by a resistance is given by any of the following formulas:
- Power consumed by R1 is given by:

$$P_{R1} = V_{R1} \times I_{R1} = 12V \times 6mA = 72 \text{ mW.}$$

$$P_{R1} = \frac{V_{R1}^2}{R1} = \frac{12V^2}{2K\Omega} = \frac{144}{2K\Omega} = 72 \text{ mW.}$$
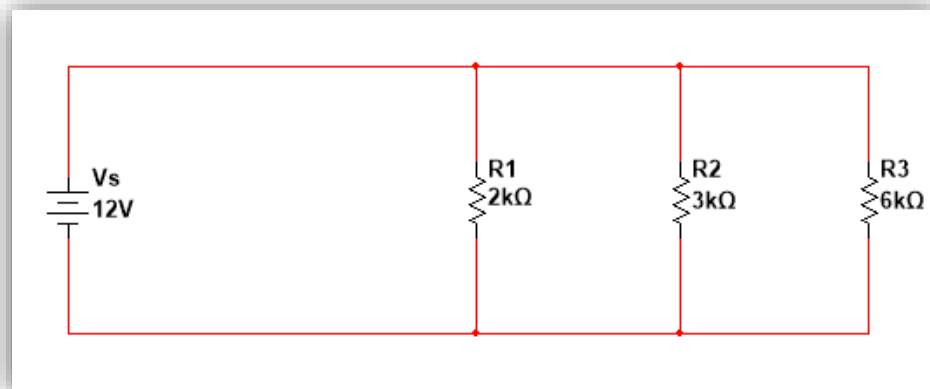
$$P_{R1} = I_{R1}^2 \times R1 = (6mA)^2 \times 2K\Omega = 36 \mu \times 2K\Omega = 72 \text{ mW.}$$




# Parallel Circuit Example

- For the following Circuit find:
  - d- Find the power consumed by R1, R2 & R3.
- The Power consumed by a resistance is given by any of the following formulas:
- Power consumed by R2 is given by:

$$P_{R2} = V_{R2} \times I_{R2} = 12V \times 4mA = 48 \text{ mW.}$$

$$P_{R2} = \frac{V_{R2}^2}{R2} = \frac{12V^2}{3K\Omega} = \frac{144}{3K\Omega} = 48 \text{ mW.}$$
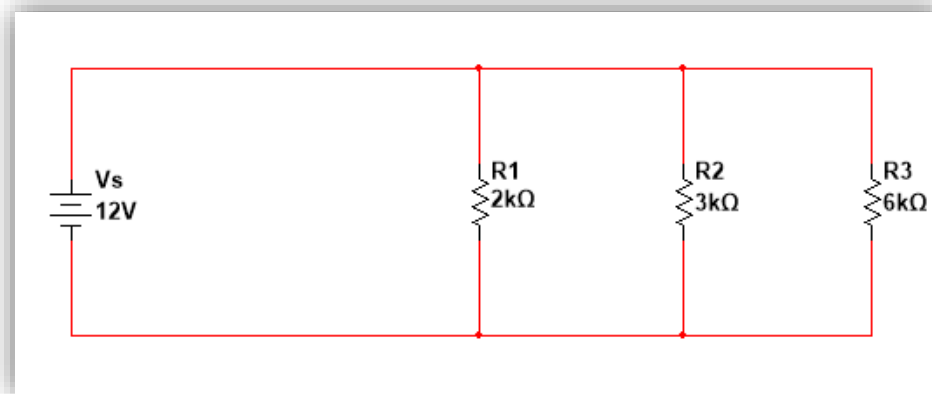
$$P_{R2} = I_{R2}^2 \times R2 = (4mA)^2 \times 3K\Omega = 16 \mu \times 3K\Omega = 48 \text{ mW.}$$




# Parallel Circuit Example

- For the following Circuit find:
  - d- Find the power consumed by R1, R2 & R3.
- The Power consumed by a resistance is given by any of the following formulas:
- Power consumed by R3 is given by:

$$P_{R3} = V_{R3} \times I_{R3} = 12V \times 2mA = 24 \text{ mW.}$$

$$P_{R3} = \frac{V_{R3}^2}{R3} = \frac{12V^2}{6K\Omega} = \frac{144}{6K\Omega} = 24 \text{ mW.}$$
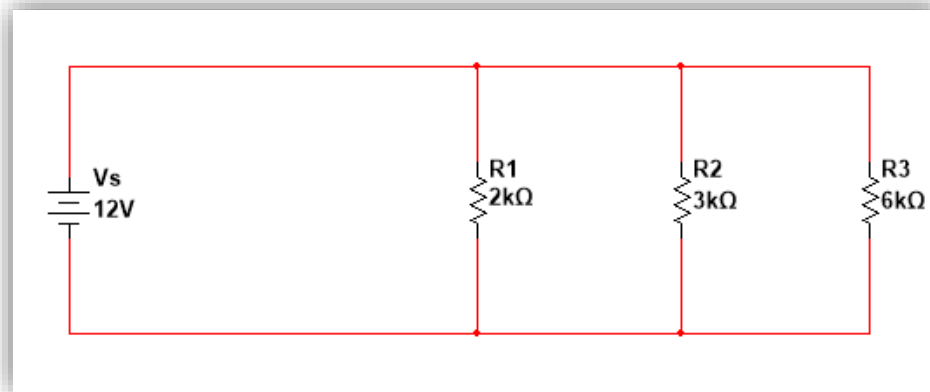
$$P_{R3} = I_{R3}^2 \times R3 = (2mA)^2 \times 6K\Omega = 24 \text{ mW.}$$




# Parallel Circuit Example

- For the following Circuit find:
  - e- Find the power delivered by the voltage source.

Power delivered by the voltage source is always equal to the sum of the powers consumed by the individual resistances. Therefore:

Power Delivered =  $P_{R1} + P_{R2} + P_{R3} = 72 \text{ mW} + 48 \text{ mW} + 24 \text{ mW} = 144 \text{ mW}$  which is the power delivered by the voltage source.

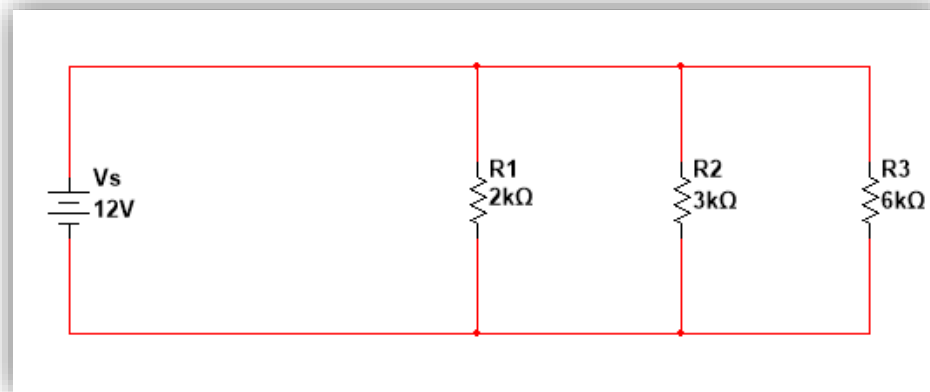Another way of finding the power delivered by the voltage source is obtained using the formula:  
 $P_s = V_s \times I_s = V_s \times I_T = 12\text{V} \times 12 \text{ mA} = 144 \text{ mW}.$




# Kirchhoff's Current Law, KCL

- Kirchhoff's Current Law (KCL) Can be stated as one of the following:
- the algebraic sum of the currents entering a point (node) is equal to the sum of the currents leaving that same point (node).
- If all currents are entering a point (node), their sum will be equal to 0.
- If all currents are leaving a point (node), their sum will also be equal to 0.
- Where a Node is an electrical point connecting two or more elements
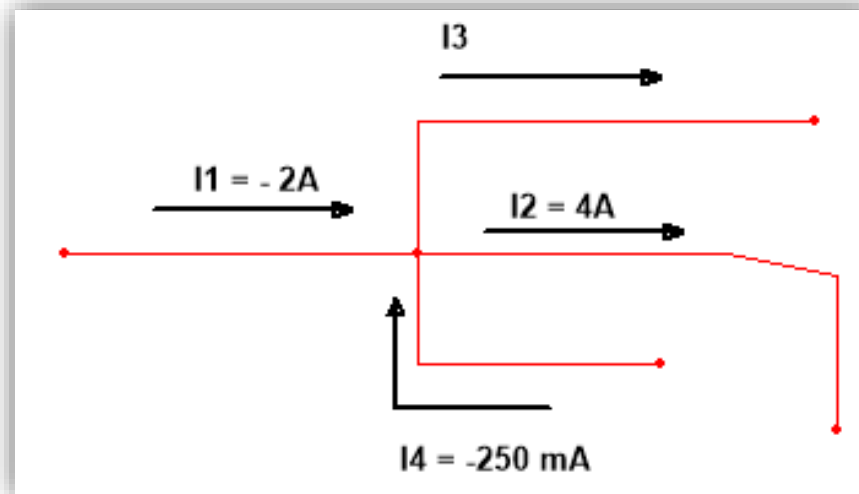
# Kirchhoff's Current Law, KCL Example

- For the following circuit, what is the value of  $I_3$ ?
- Based on KCL, the sum of all currents entering a node is equal to the sum of all currents leaving that node. Therefore:
  - $I_1 + I_4 = I_2 + I_3$
  - $I_3 = I_1 + I_4 - I_2$
  - $I_3 = -2A + (-250\text{ mA}) - 4A = -6.25A$



# Current Division Formula

- Current division only applies to a parallel combination of components.
- A total current  $I_T$  entering a node that contain n parallel resistances, will be divided between the resistances based on the following formula:
- $I_{Rx} = I_T \times \frac{R_T}{R_x}$ , Where  $x = 1, 2, 3, \dots, n$ , where  $R_T$  is the total resistance of the parallel branch. Therefore:

- $I_{R1} = I_T \times \frac{R_T}{R_1}$

- $I_{R2} = I_T \times \frac{R_T}{R_2}$

- $I_{R3} = I_T \times \frac{R_T}{R_3} \dots$

- $I_{Rn} = I_T \times \frac{R_T}{R_n}$



# Current Division Formula Example

- Find the values of  $I_{R1}$ ,  $I_{R2}$  and  $I_{R3}$  for the following parallel combination using the current division formula and verify KCL.


- $I_{Rx} = I_T \times \frac{R_T}{R_x}$ , where  $x = 1, 2, 3, \dots, n$ , Therefore:

- $R_T = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)} = \frac{1}{\left(\frac{1}{2K} + \frac{1}{3K} + \frac{1}{6K}\right)} = 1K\Omega$

- $I_{R1} = I_T \times \frac{R_T}{R_1} = 12 \times \frac{1K\Omega}{2K\Omega} = 6 \text{ mA}.$

- $I_{R2} = I_T \times \frac{R_T}{R_2} = 12 \times \frac{1K\Omega}{3K\Omega} = 4 \text{ mA}.$

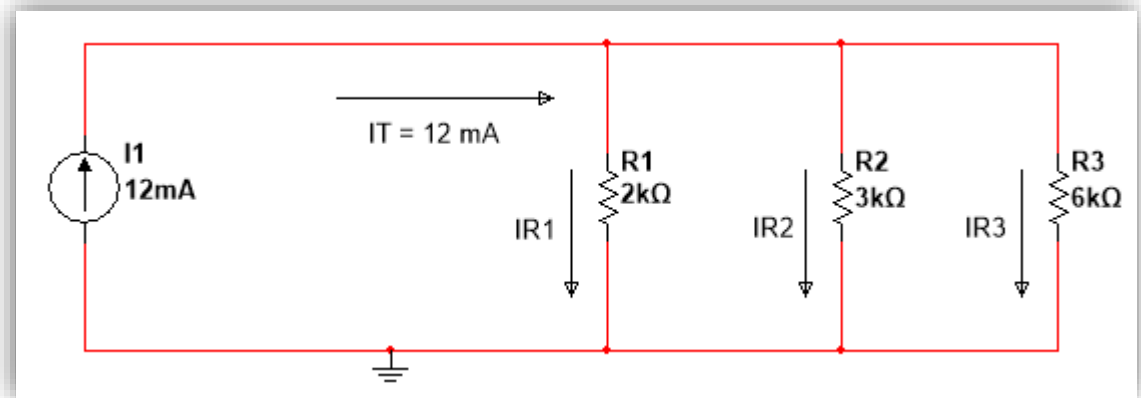- $I_{R3} = I_T \times \frac{R_T}{R_3} = 12 \times \frac{1K\Omega}{6K\Omega} = 2 \text{ mA}.$




# Current Division Formula Example

- Find the values of  $I_{R1}$  ,  $I_{R2}$  and  $I_{R3}$  for the following parallel combination using the current division formula and verify KCL.

- Verifying KCL:
- KCL states that the sum of currents entering a node is equal to the sum leaving that same node. From the circuit shown:
- There is only one current entering Node A which is the total current and it is  $I_T$  and it is equal to 12 mA.
- The currents leaving node A are:  $I_{R1} = 6 \text{ mA}$ ,  $I_{R2} = 4 \text{ mA}$  &  $I_{R3} = 2 \text{ mA}$ .


$$I_{R1} + I_{R2} + I_{R3} = 6 \text{ mA} + 4 \text{ mA} + 2 \text{ mA} = 12 \text{ mA} \text{ which is the value of } I_T = 12 \text{ mA}$$

- This verifies KCL.

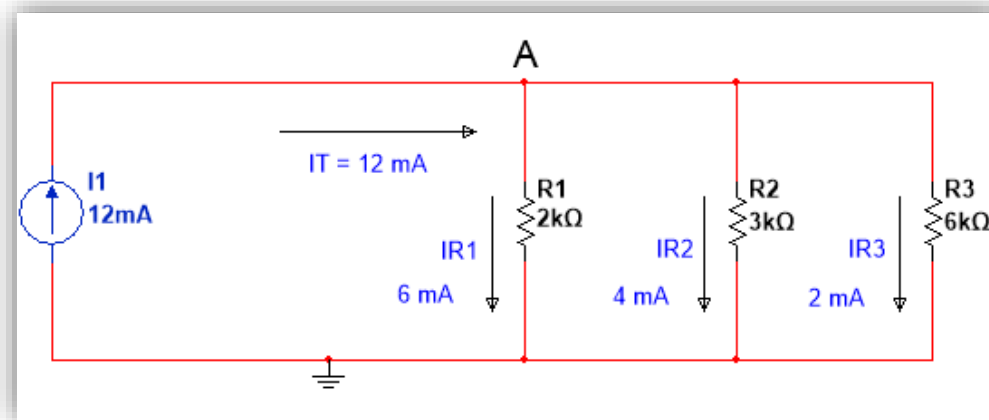
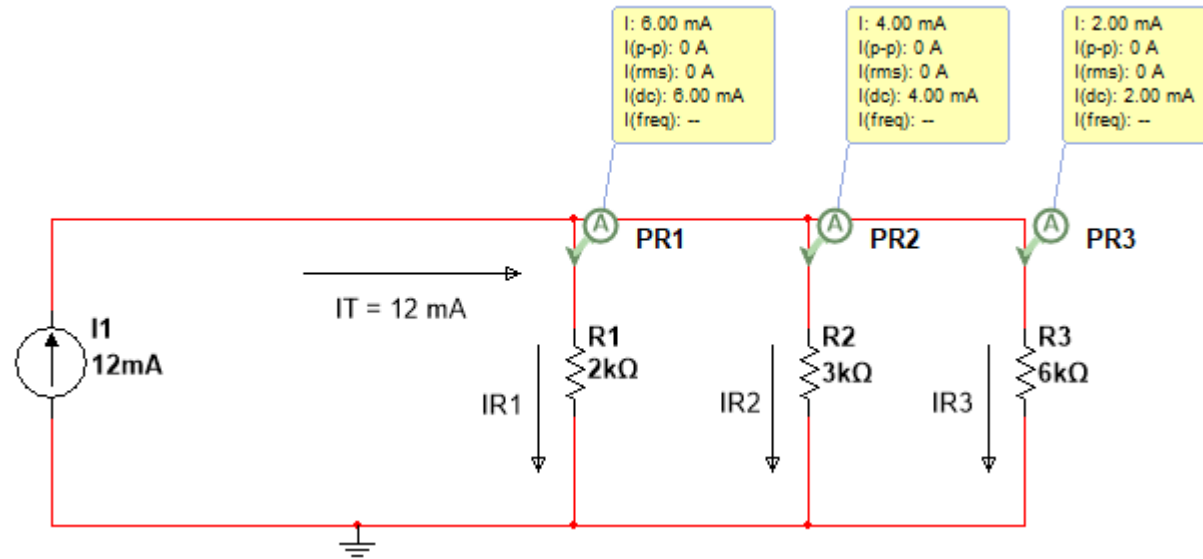
# Current Division Formula Example

- Using MultiSim, the simulation for the parallel circuit yields:



This Concludes The Parallel Resistive Circuits PPT