RC circuits under AC

## **Trigonometric Function arguments**

- The argument of the sine or cosine waveforms or any trigonometric function is always an angle even though it may appear that it is a function of time. See the following:
  - $\omega t = 2\pi F t$ .  $\omega$  is the angular frequency in radians and F is the frequency in Hz.

• 
$$F = \frac{1}{T \text{ in seconds}}$$

Therefore:

• 
$$\omega t = 2\pi Ft = 2(\pi \text{ in radians}) \times \frac{(t \text{ in seconds})}{(T \text{ in seconds})} = \frac{2\pi t}{T}$$
 Radians

## **Complex Numbers Review**

- Under AC conditions, the capacitor behaves as an ohmic value which is known as the capacitive reactance  $X_c$ .
- Such a reactance is manifested as an imaginary number.
- That coupled with the fact that resistances are considered real values dictates that a total ohmic value that encompasses resistances and capacitances will end up as a complex number.
- A complex number can be represented in 2 formats:
  - Rectangular format as Z = a + jb (where j indicates the imaginary number).
  - Polar Format as  $Z = |Z| \angle \theta$  which is a magnitude at a certain angle.

# **Complex Number Conversions**

- Given a complex number represented in the 2 formats:
  - Rectangular format as Z = a + jb (where j indicates the imaginary number).
  - Polar Format as  $Z = |Z| \angle \theta$  which is a magnitude at a certain angle.
- To convert from rectangular to polar:
  - $|Z| = \sqrt{a^2 + b^2}.$
  - $\angle \theta = Tan^{-1}\left(\frac{|b|}{a}\right).$
- To convert from polar to rectangular:
  - The real part is given by:
    - $a = |Z| \times \cos(\theta)$
  - The imaginary part is given by
    - $\mathbf{b} = |\mathbf{Z}| \times \sin(\theta)$
- Additions & Subtractions are easier done in rectangular format.
- Divisions & Multiplications are easier done in polar format.

Complex Number Addition, Subtraction, Multiplication & Division

- Given 2 complex numbers:
  - $Z_1 = a_1 + j \ b_1 = |Z_1| \angle \theta_1 \& Z_2 = a_2 + j \ b_2 = |Z_2| \angle \theta_2$

Then :

For additions and subtractions:

- $Z_1 + Z_2 = (a_1 + a_2) + j(b_1 + b_2)$
- $Z_1 Z_2 = (a_1 a_2) + j(b_1 b_2)$
- For multiplications and divisions:
- $Z_1 \times Z_2 = |Z_1| \angle \theta_1 \times |Z_2| \angle \theta_2 = |Z_1| \times |Z_2| \angle (\theta_1 + \theta_2)$  (Multiply the magnitudes and add the angles).
- $\frac{|Z_1| \ge \theta_1}{|Z_2| \ge \theta_2} = \frac{|Z_1|}{|Z_2|} \ge (\theta_1 \theta_2)$  (Divide the magnitudes and subtract the denominator angle from the numerator angle).

## Voltage and Current Relationship in a Capacitor

- The capacitor will always try to oppose a change in the voltage across it by briefly holding its value.
- The capacitor will never oppose a current change through it.
- Because of the above two facts, the voltage across the capacitor will be held behind the current through the capacitor.
- In other words, we say that the capacitor voltage **lags** the current through it, or also stated as the current through the capacitor **leads** the voltage across it.
- The capacitor voltage will always lag the current through it by 90 deg. Stated otherwise, the current through the capacitor will lead the voltage across it by 90 deg.

#### The "ELI the ICE man" Memory Aid

- L is the inductor
- C is the capacitor
- E is the voltage
- I is the current
- Always the phase difference is 90°.
- •ELI means in an inductor L; the voltage E across it leads the current through it by 90°.
- •ICE means in a capacitor C, the current I through it leads the voltage E across it by 90°.

## The Capacitive Reactance (Impedance) Xc



- The capacitive reactance of a capacitance C in an AC circuit with a frequency F is given by:
  - $X_C = \frac{1}{2\pi FC} = \frac{1}{\omega C}$  is the magnitude of the capacitive reactance.
  - Since  $\omega = 2\pi F$ ,  $\omega$  is the angular frequency and F is the frequency.
- Since it is an imaginary value, it is expressed as:
  - $-jX_C$  in rectangular format &
  - $|X_C| \ge -90$  Deg in Polar format.
- Expressed in time domain, this would be:
  - $X_C(t) = |X_C| \sin(\omega t 90) = \frac{1}{2\pi FC} \sin(\omega t 90).$
- In a capacitor, always the voltage across the capacitor lags the current through it by 90°.

# Series RC circuits under AC



## Series RC Circuits Under AC Equations

- For the series RC circuit shown:
- Vs (t) = Vp × sin ( $2\pi$ Ft) = Vp × sin ( $\omega$ t) = Vp  $\angle 0$  deg



- The magnitude value of the capacitive reactance is given by:  $X_C = \frac{1}{2\pi FC}$ .
- Since this is a series circuit, the total impedance seen by the voltage source  $Z_T$  is the sum of both R & Xc (not algebraically) and it is given by:
- $Z_T = R jX_C$ , represented in rectangular format.
- $Z_T = |Z_T| \angle \theta$  represented in polar format where:
  - $|Z_T| = \sqrt{R^2 + Xc^2}$  for the magnitude of the polar form.
  - $\theta = \tan^{-1}(\frac{-Xc}{R})$  for the phase angle for the polar form.
- This angle indicates that the total current  $I_T$  is leading the total voltage  $V_S$  by a value of  $|\theta|$ . This is always the case in a capacitive circuit.

### Series RC Circuits Under AC Equations Continued

- The total current  $I_T$  For the series RC is given by:
  - $I_T = \frac{V_T}{Z_T} = \frac{V_S}{Z_T}$
  - $I_T = I_R = I_C$
- The voltage across the resistance is given by:
  - $V_R = I_R \times R = I_T \times R$
  - The voltage across a resistance and the current through it are in phase.
- The voltage across the capacitor is given by:
  - $V_C = I_C \times X_C = I_T \times X_C$
  - The voltage across the capacitor and the current through it are  $90^{\circ}(\frac{\pi}{2})$  out of phase; with the current through the capacitor leading the voltage across it.
- The total applied voltage to the R-C series combination in terms of the voltages across R and across C is given by:

• 
$$V_T = \sqrt{V_R^2 + V_C^2}$$

- For this series RC circuits under AC conditions, all currents and voltages are merely AC waveforms.
- To plot those sine waves vs time, it might be a bit cluttered to see the phase relationship between all those waveforms.
- It may be even much harder for an AC circuit to represent on a plot especially if the circuit becomes more complex and not merely a series RC circuit.
- Recall that the series current leads the source voltage by a value of  $\theta$  and the current through the cap which is in phase with the voltage across the resistance leads the voltage across the cap by 90°.
- Phasor diagram solve this issue by simply representing the sine waves as arrows that represent the peak value and the phase angle.

• The following figure shows a plot of the 3 sine waves,  $V_S$  (Yellow),  $V_R$  (Red) and  $V_C$  (Green).



• For this series RC circuits under AC conditions, to draw the phasor diagram look for a signal that is common to all elements. That would the current through the circuit. This current would be used as the reference signal.



• Since the voltage across R is in phase with the current through R, then they should line up as shown.



• Since the voltage across the capacitor lags the current through it by 90°, then it would be drawn as orthogonal to the current in a manner that is lagging by 90° as shown.



• Based on KVL, the source voltage is the sum of the voltage across R and the voltage across C. It would be represented as their vector sum and is drawn as shown on the phasor diagram.



• Notice that the total current leads the total voltage by an angle of  $\theta$  which is the case in a series RC circuit.

- It is to note that each arrow represent a sine wave in the time domain:
  - $V_S(t) = V_{S-peak} \times \sin(\omega t \theta)$ •  $I_S(t) = I_{S-peak} \times \sin(\omega t)$ •  $V_R(t) = V_{R-peak} \times \sin(\omega t)$ •  $V_C(t) = V_{C-peak} \times \sin(\omega t - 90^\circ)$  $I_T = I_R = I_C = I_{source}$  $V_R$ V<sub>C</sub>

## Series RC Circuits Under AC Example

- For the following circuit find:
  - a)  $X_C$  both in rectangular and polar forms.
  - b)  $Z_T$  seen by the voltage source, both in polar & rectangular forms.
  - c)  $I_T$ ,  $V_R$ ,  $V_C$  and the phase difference between  $V_S \& I_T$ .
  - d) Verify that the total voltage  $V_S$  is the sum of  $V_R \& V_C$  (not the algebraic sum).
  - e) Draw the phasor diagram showing the total current and all voltages.



## Series RC Circuits Under AC Example Solution

#### • Solution:

- a)  $X_C$  both in rectangular and polar forms.
  - $X_C = 1/2\pi FC = 1/(2\pi \times 1 \text{ KHz} \times 0.1 \text{ uF}) = 1591\Omega = 1.59 \text{ K}\Omega$ . Magnitude value.
    - In rectangular format it is –j 1.59 KΩ.
    - In Polar Format it is 1.59 K $\Omega \geq -90^{\circ}$
- *b)* Z<sub>T</sub> both in polar & rectangular forms. Since the resistance and the capacitance are in series, the total impedance is given by their sum (not algebraic sum, because R is real and Xc is imaginary)

In rectangular format:

•  $Z_T = R - jXc = 1K - j1.59K$ 

#### In polar format:

- $|Z_T| = \sqrt{R^2 + Xc^2} = \sqrt{1K^2 + (-1.59K)^2} = \sqrt{3.528} = 1.88 \text{ K}\Omega \text{ Magnitude.}$
- $\theta = \tan^{-1}(\frac{-|Xc|}{R}) = \theta = \tan^{-1}(\frac{-1.59}{1}) = -57.83^{\circ}$ . Which is Always the Phase Angle between the voltage source and the total current IT.

## Series RC Circuits Under AC Example Solution Continued

- Solution:
  - c)  $I_T$ ,  $V_R$ ,  $V_C$  and the phase difference between  $V_S \& I_T$ .
    - Since divisions & multiplications are easier performed in polar format:

• 
$$I_T = \frac{\text{Peak of } V_S \angle 0}{Z_T \text{ in polar Format}} = \frac{V_P}{|Z_T|} = \frac{V_P v}{|Z_T| \angle 0} = \frac{6 \angle 0}{1.88 \angle -57.83^\circ} = 3.19 \text{ mA} \angle 57.83^\circ$$

- In time domain  $I_T(t) = 3.19 \text{ mA} \sin(2\pi Ft + 57.83^\circ)$
- Since this is a series circuit  $I_T = I_R = I_C = 3.19 \text{ mA} \ge 57.83^\circ$  Therefore:
- $V_R = I_R \times R = 3.19 \text{ mA} \ge 57.83^\circ \times 1 K\Omega = 3.19 V \ge 57.83^\circ$
- In time domain  $V_R(t) = 3.19 V \sin(2\pi F t + 57.83^\circ)$
- $V_C = I_C \times X_C = 3.19 \text{ mA} \ge 57.83^\circ \times 1.59 \text{ K}\Omega \ge -90^\circ = 5.07 \text{ V} \ge (57.83^\circ 90^\circ) = 5.07 \text{ V} \ge -32.17^\circ$
- In time domain  $V_C(t) = 5.07 V \sin(2\pi F t 32.17^\circ)$
- Notice that the difference between the current through C and the voltage across it is  $[57.83^{\circ} (-32.17^{\circ}) = 90^{\circ}]$  with the current leading the voltage.
- Since  $V_s$  is at 0° phase angle and the current is at 57.83°, then the current leads the voltage source by 57.83°. This enforces the fact that in a capacitive circuit, the total current leads the voltage source by  $\theta$ .

Series RC Circuits Under AC Example Solution Continued

• Solution:

d) Verify that the total voltage  $V_S$  is the sum of  $V_R \& V_C$ .

• The total applied voltage to the R-C series combination in terms of the voltages across R and across C is given by:

• 
$$V_T = \sqrt{{V_R}^2 + {V_C}^2}$$
  
•  $V_T = \sqrt{(3.19)^2 + (5.07)^2} \approx 6 V$ 

#### Series RC Circuits Under AC Example Solution Continued

e) Draw the phasor diagram showing the total current and all voltages.

$$V_R 3.19 V$$
  $I_T = I_R = I_C = I_{source} = 3.19 mA$   
 $\theta = 57.83^{\circ}$   
 $V_C = 5.07 V$   
 $V_S = 6V$ 

• Notice that the total current leads the total voltage by an angle of  $\theta = 57.83^{\circ}$  which is the case in a series RC circuit.

Parallel RC circuits under AC

# Parallel RC circuits under AC



### Parallel RC Circuits Under AC Equations

- For the series RC circuit shown:
- $Vs = Vp \times sin (2\pi Ft) = Vp \angle 0 deg$



- The magnitude value of the capacitive reactance is given by:  $X_C = \frac{1}{2\pi FC}$ .
- Since this is a parallel circuit, the total impedance seen by the voltage source Z is the product of both R & Xc divided by their sum (not algebraically) and it is given by:
- $Z_T = \frac{R \times (-jX_C)}{R jX_C}$ , represented in rectangular format.
- $Z_T = |Z_T| \ge \theta$  represented in polar format where:
  - $|Z_T| = \frac{R \times X_C}{\sqrt{R^2 + Xc^2}}$  for the magnitude for the polar form.
  - $\theta = \tan^{-1}(\frac{R}{Xc})$  for the phase angle for the polar form.
- This angle indicates that the total current  $I_T$  is leading the total voltage  $V_S$  by a value of  $|\theta|$ . This is always the case in a capacitive circuit.

## Series RC Circuits Under AC Equations Continued

- The total current  $I_T$  For the parallel RC is given by:
  - $I_T = \frac{V_T}{Z_T} = \frac{V_S}{Z_T}$
  - $V_s = V_R = V_C$
- The current through the resistance is given by:
  - $I_R = \frac{V_R}{R}$
  - The voltage across a resistance and the current through it are in phase.
- The current through the capacitor is given by:
  - $I_C = \frac{V_C}{X_C}$
  - The voltage across the capacitor and the current through it are  $90^{\circ}(\frac{\pi}{2})$  out of phase with the current through the capacitor leading the voltage across it.
- The total current  $I_T$  sourced by the voltage source in terms of the resistance and the capacitance current is given by:

• 
$$I_T = \sqrt{{I_R}^2 + {I_C}^2}$$

• For this parallel RC circuits under AC conditions, to draw the phasor diagram look for a signal that is common to all elements. That would the voltage across all elements  $V_s$ ,  $V_R$  and  $V_C$ , in the circuit. This voltage would be used as the reference signal.



• Since the current through R is in phase with the voltage across it, then they should line up as shown.



• Since the current through the capacitor leads the voltage across it by 90°, then it would be drawn as orthogonal to the voltage across it in a manner that is leading by 90° as shown.



• Based on KCL, the source current is the sum of the currents through R and C. It would be represented as their vector sum and is drawn as shown on the phasor diagram.



• Notice that the total current leads the total voltage by an angle of  $\theta$  which is the case in a series RC circuit.

• It is to note that each arrow represent a sine wave in the time domain:



• Notice that the peaks of the voltages for all 3 elements are equal:

• 
$$V_{S-peak} = V_{R-peak} = V_{C-peak}$$

### Parallel RC Circuits Under AC Example

- For the following circuit find:
  - a)  $X_C$  both in rectangular and polar forms.
  - b)  $Z_T$  seen by the voltage source, both in polar & rectangular forms.
  - c)  $I_T$ ,  $I_R$ ,  $I_C$  and the phase difference between  $V_S \& I_T$ .
  - d) Verify that the total current  $I_T(I_S)$  is the sum of  $I_R \& I_C$  (not the algebraic sum).
  - e) Draw the phasor diagram showing the total voltage and all currents.



### Parallel RC Circuits Under AC Example Solution

- Solution:
- a)  $X_C$  both in rectangular and polar forms.
- $X_C = \frac{1}{2\pi FC} = \frac{1}{2\pi \times 1 \ KHz \times 0.1 \ \mu F} = 1.59 \ K\Omega.$ 
  - In rectangular format it is  $-j 1.59 \text{ K}\Omega$ .
  - In Polar Format it is 1.59 K $\Omega \geq -90^{\circ}$

b)  $Z_T$  both in polar & rectangular forms. Since the resistance and the capacitance are in parallel, the total impedance is given:

• In rectangular format:

$$Z_T = \frac{R \times (-jX_C)}{R - jX_C} = \frac{1 \times (-j1.59)}{1 - j1.59} = \frac{-j1.59}{1 - j1.59} = \frac{-j1.59(1 + j1.59)}{(1 - j1.59)(1 + j1.59)} = \frac{2.52 - j1.59}{3.53} = 0.712 - j0.45$$

- In polar format, simply convert the rectangular format to its polar format to obtain:
  - $|Z_T| = \sqrt{0.713^2 + 0.45^2} = 0.846$ •  $\theta = tan^{-1} \left(\frac{-045}{0.712}\right) = -32.16^\circ$
- We could have also found the polar format values using:

• 
$$|Z_T| = \frac{R \times X_C}{\sqrt{R^2 + X_C^2}} = \frac{1 \times 1.59}{\sqrt{1^2 + 1.59^2}} = 0.846$$
  
•  $\theta = \tan^{-1}(\frac{-R}{X_C}) = \tan^{-1}(\frac{-1}{1.59}) = -32.16^{\circ}$ 

• Which is Always the Phase Angle between the voltage source and the total current  $I_T$ .

#### Parallel RC Circuits Under AC Example Solution

- c) Find  $I_T$ ,  $I_R$ ,  $I_C$  and the phase difference between  $V_S \& I_T$ .
- Since this is a parallel circuit, then:  $V_S = V_R = V_C = 6 \angle 0^\circ V$ .
- The total current  $I_T$  is equal to the total voltage divided by the total impedance  $Z_T$ .

$$I_T = \frac{V_s}{Z_T} = \frac{6\angle 0^\circ}{0.846 \ K\Omega \angle -32.16} = 7.09 \angle 0 - (-32.16) = 7.09 \angle 32.16 \ mA$$

- The current through the resistance is equal to  $\frac{V_R}{R} = \frac{6 \angle 0^\circ}{1K\Omega} = 6 \ mA$  The current through the capacitor is equal to  $\frac{V_C}{X_C} = \frac{6 \angle 0^\circ}{1.59 \ K\Omega \angle -90^\circ} = 3.77 \ \angle -90^\circ \ mA$
- The phase difference between  $V_T$  and  $I_T$  is equal to  $\theta = 32.16$  with the total current leading the total voltage.

d) Verify that the total voltage  $I_S$  is the sum of  $I_R \& I_C$  (not the algebraic sum).

• To verify that the total current  $I_S$  is equal to the sum of  $I_R \& I_C$ , use:

• 
$$I_T = \sqrt{I_R^2 + I_C^2} = \sqrt{6 m A^2 + 3.77 m A^2} = 7.09$$
 which is what  $I_T$  is equal to.

e) Draw the phasor diagram showing the total voltage and all currents.



• Notice that the total current leads the total voltage by an angle of  $\theta$ .

## **Conversion From Parallel To Series Form**

- A parallel *RC* circuit which has a  $Z_T$  with a phase angle  $\theta$ , can be converted into a series  $R_1C_1$  circuit by using the following formulas:
- $Z_T = \frac{R \times X_C}{\sqrt{R^2 + X_C^2}}$  is the total impedance of the parallel circuit.
- $\theta = \tan^{-1}(\frac{R}{Xc})$  is the phase angle between the total current and the total voltage.
- $R_1 = Z_T \times Cos(\theta)$
- $X_{c1(equ)} = Z_T \times Sin(\theta)$
- Such equations can be used to make the analysis of a series-Parallel RC circuit easier.



#### Parallel to Series Conversion Example

• Convert the following circuit into its series equivalent.



#### Parallel to Series Conversion Example

• Convert the following circuit into its series equivalent Solution:



- From a previous example, the total impedance and its phase angle were calculated as:
  - $|Z_T| = \frac{R \times X_C}{\sqrt{R^2 + X_C^2}} = \frac{1 \times 1.59}{\sqrt{1^2 + 1.59^2}} = 0.846.$ •  $\theta = \tan^{-1}(-\frac{R}{X_C}) = \tan^{-1}(-\frac{1}{1.59}) = -32.16^{\circ}.$
- Therefore:
- $R_1 = Z_T \times Cos(\theta) = 0.846 \times Cos(-32.16) = 0.72$
- $Xc_{1(equ)} = Z_T \times Sin(\theta) = 0.846 \times Sin(-32.16) = -0.45$



## **RC** Circuits Analysis Main Concepts

- Any component in the RC circuit under AC can be thought of as a complex number.
- A resistance is a real component designated as R, but it can be thought of as a complex number with a zero imaginary part such as: Z = R + j0.
- A capacitor is an imaginary component designated as  $jX_c$ , but it can be thought of as complex number with a zero real part such as  $Z = 0 jX_c$ .
- In fact, an RC circuit under AC can be completely analyzed with complex number arithmetic and then each component whether an impedance, current, voltage, power or energy can be converted back to the time domain.
- All circuit analysis rules and laws apply the same, such as ohm's law, KVL, KCL, voltage division, current division etc...
- The symbol "||" will be used to indicate a parallel combination.

• For the following circuit find:

a)  $X_{C1}, X_{C2}$ .

b)  $Z_T$  seen by the voltage source  $V_s$ .

c)  $I_T$ ,  $I_{R1}$ ,  $I_{C1}$ ,  $V_{R1}$ ,  $V_{C1}$ ,  $I_{R2}$ ,  $I_{C2}$ ,  $V_{R2}$  and  $V_{C2}$  and the phase difference between  $V_S \& I_T$ . d) Verify that the KVL applies by verifying that the sum of  $V_{R1}$ ,  $V_{C1}$  and  $V_{R2}$  or  $V_{C2}$  is equal to the total voltage  $V_S$ 







#### **b)** $Z_T$ seen by the voltage source $V_s$ :

- $Z_T$  is the series combination of R1,  $X_{C1}$  and  $R2||X_{C2}$ . Therefore:
- $Z_T = R1 + X_{C1} + R2||X_{C2}||$
- $Z_T = 0.5 \ K\Omega \ -j \ 0.795 \ K\Omega \ +1 \ K\Omega \ || \ (-j1.59 \ K\Omega)$
- Recall that when there are 2 elements in parallel, their equivalent will be their product divided by their sum. Therefore:

• 
$$Z_T = 0.5 \ K\Omega \ -j \ 0.795 \ K\Omega \ + (\frac{1K \times -j1.59}{1K \ -j1.59})$$

- Using complex number arithmetic such as multiplying by the conjugate results in:
- $Z_T = 0.5 K\Omega j 0.795 K\Omega + (0.72 j0.45)$
- $Z_T = 1.22 K\Omega j 1.245$
- $Z_T$  expressed in polar format is  $Z_T = 3.03 \text{ K}\Omega \ge -45.58^\circ$





c)  $I_T$ ,  $I_{R1}$ ,  $I_{C1}$ ,  $V_{R1}$ ,  $V_{C1}$ ,  $I_{R2}$ ,  $I_{C2}$ ,  $V_{R2}$  and  $V_{C2}$  and the phase difference between  $V_S \& I_T$ 

- $I_T = \frac{V_T}{Z_T} = \frac{6V}{1.22 K\Omega j \ 1.245}$ . Using Complex numbers arithmetic and multiplying by the conjugate, such as: •  $I_T = \frac{6V}{1.22 K\Omega - j \ 1.245} \times \frac{1.22 K\Omega + j \ 1.245}{1.22 K\Omega + j \ 1.245}$ 
  - In rectangular format:
  - $I_T = (2.41 + j \ 2.45) \text{ mA}$
  - In polar format:  $I_T = 3.43 \text{ mA} \checkmark +45.47$
- The values of  $I_{R1}$  and  $I_{C1}$  are given by:  $I_{R1} = I_{C1} = I_T = (12.41 + j \ 2.45) \text{ mA} = 3.43 \text{ mA} \angle +45.47$

- c)  $V_{R1}$ ,  $V_{C1}$ ,  $I_{R2}$ ,  $I_{C2}$ ,  $V_{R2}$  and  $V_{C2}$  and the phase difference between  $V_S \& I_T$
- $V_{R1} = I_{R1} \times R_1 = (2.41 + j \ 2.45) \text{ mA} \times 0.5 \ K\Omega$ 
  - In rectangular format:
  - $V_{R1} = 1.205 + j1.225$
  - In Polar Format:
  - $V_{R1} = 1.715 \ \angle +45.47$
- $V_{C1} = I_{C1} \times X_{C1} = (2.41 + j \ 2.45) \text{ mA} \times (-j0.795 \ K\Omega)$ 
  - In rectangular format:
  - $V_{C1} = (1.95 j1.91) V$
  - In Polar Format:
  - $V_{C1} = 2.72 \ge -44.53 \text{ V}$

c)  $I_{R2}$ ,  $I_{C2}$ ,  $V_{R2}$  and  $V_{C2}$  and the phase difference between  $V_S \& I_T$ 

- The values of the currents through  $R_2$  and  $C_2$  can be found either by:
  - Using the current division rule where the total current  $I_T$  is divided between and  $R_2$  and  $X_{C2}$ .
  - Or:
  - By finding the voltage between points A & B,  $V_{AB}$  which is effectively the voltage across the parallel combination of  $R_2$  and  $X_{C2.}$ . Once that is found, Ohm's law can be used to find the currents. The latter method will be used.
- Using ohm's law, the voltage across the parallel combination of  $R_2$  and  $X_{C2}$  is calculated by multiplying the total current  $I_T$  by the impedance between points A & B. The impedance between points A & B is shown in the following and it is equal to the series combination of  $R = 0.72 K\Omega$  and  $X_{C2} = 0.45 K\Omega$  and that is  $(0.72 j \ 0.45)K\Omega$ .



- c)  $V_{R2}$  and  $V_{C2}$  and the phase difference between  $V_S \& I_T$
- $V_{AB} = I_T \times (R + X_C) = (2.41 + j \ 2.45) \text{ mA} \times (0.72 \ K\Omega j \ 0.45 \ K\Omega)$
- $V_{AB} = 1.73 j1.0845 + j1.76 + 1.10 = 2.83 + j0.6755$  in rectangular format.
- $V_{AB} = 2.91 \angle 13.42$  °V in polar format.
- Since the voltage between point A & B is the same as the voltage across R2 and C2, then:
- $V_{AB} = V_{R2} = V_{C2} = 2.83 + j0.6755 = 2.91 \angle 13.42$  °V.



c)  $I_{R2}$ ,  $I_{C2}$ , and the phase difference between  $V_S \& I_T$ 

• 
$$I_{R2} = \frac{V_{R2}}{R2} = \frac{2.83 + j0.6755}{1 \text{ K}\Omega} = (2.83 + j0.6755) \text{ } mA = 2.91 \angle 13.42^{\circ} \text{ } mA.$$
  
•  $I_{C2} = \frac{V_{C2}}{X_{C2}} = \frac{2.91 \angle 13.42^{\circ} \text{ } V}{-j1.59 \text{ } \text{ } \text{ } \Omega} = \frac{2.91 \angle 13.42^{\circ} \text{ } V}{1.59 \text{ } \text{ } \Omega \text{ } \angle -90^{\circ}} = 1.83 \angle 103.42^{\circ} \text{ } mA.$ 

• KCL can be verified by showing that  $I_T = I_{R2} + I_{C2}$  using the following formula for a total current entering a parallel combination:

•  $I_T = \sqrt{I_R^2 + I_C^2} = \sqrt{2.91^2 + 1.83^2} = 3.43 \text{ mA}$  which is the magnitude of the total current  $I_T$ .

• The phase difference between the voltage source  $V_S$  and the total current  $I_T$  is the phase angle of  $I_T$  itself which is 45.54° with the total current leading the total voltage source  $V_S$ .



d) Verify that the KVL applies by verifying that the sum of  $V_{R1}$ ,  $V_{C1}$  and  $V_{R2}$  or  $V_{C2}$  is equal to the total voltage  $V_s$ .

The voltages in the rectangular format of the voltages across all the elements in the following circuit:

- $V_{R1} = (1.205 + j1.225) V$
- $V_{C1} = (1.95 j1.91) V$
- $V_{AB} = V_{R2} = V_{C2} = (2.83 + j0.6755)V$

•  $V_S = V_{R1} + V_{C1} + V_{AB} = (1.205 + 1.95 + 2.83) + j(1.225 - 1.91 + 0.6755) = 5.99 - j0.0095 \approx 6V$ 

• This is the value of the voltage source  $V_S$ .